

Basics of Logic Design Arithmetic Logic Unit (ALU)

Computer Science 104

Today's Lecture

- Homework #3 Assigned Due Mar 4
- **Project:** form groups of 3 (preferred) by Mar 6, I will assign after that
- Project Specifications on Web, **Due April 17 (written document and demonstration)**
- Building the building blocks...

Outline

- Review
- Digital building blocks
- An Arithmetic Logic Unit (ALU)

Reading

Appendix C, Chapter 3

Review: Digital Design

- Logic Design, Switching Circuits, Digital Logic

Recall: Everything is built from transistors

- A transistor is a switch
- It is either on or off
- **On** or **off** can represent **True** or **False**

Given a bunch of bits (0 or 1)...

- Is this instruction a lw or a beq?
- What register do I read?
- How do I add two numbers?
- **Need a method to reason about complex expressions**

Review: Boolean Functions

- Boolean functions have arguments that take two values ($\{T,F\}$ or $\{0,1\}$) and they return a single or a set of ($\{T,F\}$ or $\{0,1\}$) value(s).
- Boolean functions can always be represented by a table called a "**Truth Table**"
- Example: $F: \{0,1\}^3 \rightarrow \{0,1\}^2$

a	b	c	f ₁ , f ₂
0	0	0	0 1
0	0	1	1 1
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	1	0	0 1
1	1	1	1 1

Review: Boolean Functions and Expressions


$$F(A, B, C) = (A * B) + (\sim A * C)$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Review: Boolean Gates


- **Gates** are electronics devices that implement simple Boolean functions

Examples

 


Review: Boolean Functions, Gates and Circuits

 - **Circuits** are made from a network of gates. (function compositions).



$$F = \sim a * b + \sim b * a$$


a	b	XOR(a,b)
0	0	0
0	1	1
1	0	1
1	1	0

 

Parity Example

- The parity code of a binary word counts the number of ones in a word. If there are an even number of ones the parity code is 0, if there are an odd number of ones the parity code is 1. For example, the parity of 0101 is 0, and the parity of 1101 is 1.
- Construct the truth table for a function that computes the parity of a **four-bit word**. Implement this function using AND, OR and NOT gates. (Note there are no constraints on the number of gate inputs.)

Circuit Example: Decoder

 


I_1	I_0	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Circuit Example: 2x1 MUX



Multiplexor (MUX) selects one of many inputs


 
$$MUX(A, B, S) = (A * S) + (B * \sim S)$$



Example 4x1 MUX

  

Arithmetic and Logical Operations in ISA

- What operations are there?
- Arithmetic Logic Unit (ALU)
 - Hardware that performs operations
 - Only one operation at a time
- How do we implement the operations?
 - Consider AND, OR, NOT, and ADD
 - Input is two bits, output...

Truth Table for 1-bit Addition


```

01101100
+00101100
-----
10011001
    
```

a	b	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

What is the circuit for Sum and for Cout?

A 1-bit Full Adder

 


```


01101100
+00101100
-----
10011001
    
```

a	b	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Example: 4-bit adder

 


ALU Slice (Almost)

 

Subtraction

- How do we perform integer subtraction?
- What is the HW?

ALU Slice

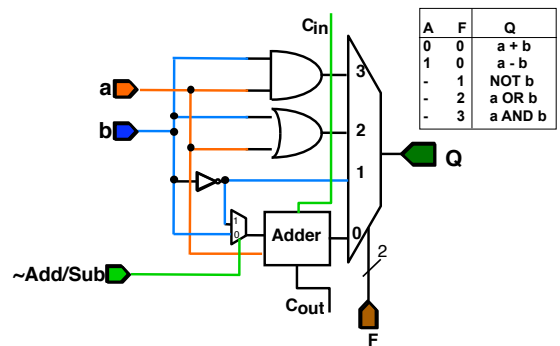

Overflow

Example1:

$$\begin{array}{r} 0100000 \\ 0110101_2 \quad (= 53_{10}) \\ +0101010_2 \quad (= 42_{10}) \\ \hline 1011111_2 \quad (= -33_{10}) \end{array}$$

Example2:

$$\begin{array}{r} 1000000 \\ 1010101_2 \quad (= -43_{10}) \\ +1001010_2 \quad (= -54_{10}) \\ \hline 0011111_2 \quad (= 31_{10}) \end{array}$$


Example3:

$$\begin{array}{r} 1100000 \\ 0110101_2 \quad (= 53_{10}) \\ +1101010_2 \quad (= -22_{10}) \\ \hline 0011111_2 \quad (= 31_{10}) \end{array}$$


Example4:

$$\begin{array}{r} 0000000 \\ 0010101_2 \quad (= 21_{10}) \\ +0101010_2 \quad (= 42_{10}) \\ \hline 0111111_2 \quad (= 63_{10}) \end{array}$$

Overflow Detection for 4-bit adder

 


The ALU

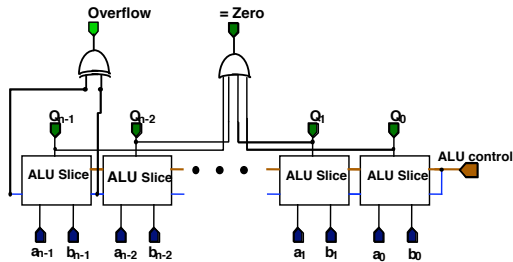

Abstraction: The ALU

 
- General structure
- Two operand inputs
- Control inputs



The Shift Operation

- Consider an 8-bit machine
- How do I implement the shift operation?

Shifter

 


Summary thus far

- Given Boolean function, generate a circuit that "realizes" the function.
 - Constructed circuits that can **add** and **subtract**.
 - The **ALU**: a circuit that can **add, subtract, detect overflow, compare, and do bit-wise operations (AND, OR, NOT)**
 - Shifter**
- Next up: Storage Elements: Registers, Latches, Buses


Memory Elements

- All the circuit we looked at so far are **combinational circuits**: the output is a Boolean function of the inputs.
- We need circuits that can remember values. (registers)
- The output of the circuit is a function of the input **AND** a stored value (state).
- Circuits with memory are called **sequential circuits**.


Set-Reset Latch

 


Set-Reset Latch (Continued)

 

Set-Reset Latch (Continued)

 

Data Latch (D Latch)

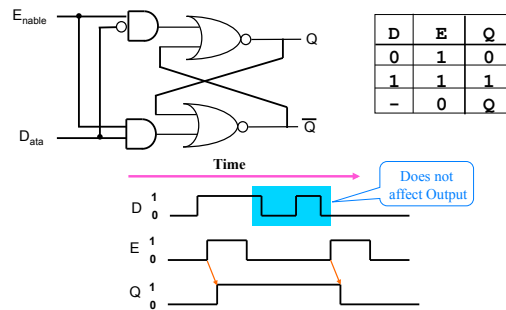

D Flip-Flop

- On C ↑ D is transferred to the first D latch and the second is stable.
- On C ↓ the output of the first stage is transferred to the second (output), and the first stage is stable.

© Alvin R. Lebeck CPS 104 31

D Flip-Flop Timing

© Alvin R. Lebeck CPS 104 32

Tri-State Driver

- The Tri-State driver is like a (one directional) switch:
 - When the Enable is on (E=1) it transfers the input to the output.
 - When the Enable is off (E=0) it disconnects the output.

D	E	Q
0	1	0
1	1	1
-	0	Z

Z :- High Impedance

© Alvin R. Lebeck CPS 104 33

Bus Connections

- The Bus: Many to many connections.
- Mutual exclusion: At most one Enable is on!

© Alvin R. Lebeck CPS 104 34

Register Cells on a bus

One can "source" and "sink" from any cell on the bus by activating the right controls (WE and RE).


© Alvin R. Lebeck CPS 104 35

3-Port Register Cell


- Stores one bit of a register
- Can Read onto Bus-A & Bus-B and Write from Bus-C Simultaneously

© Alvin R. Lebeck CPS 104 36


3-Port Register File

 

Address Decode Circuit

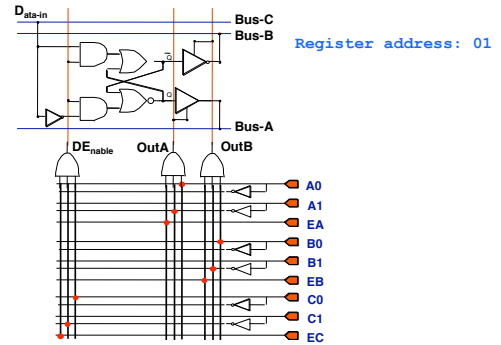

Register File (Four 4-bit Registers)

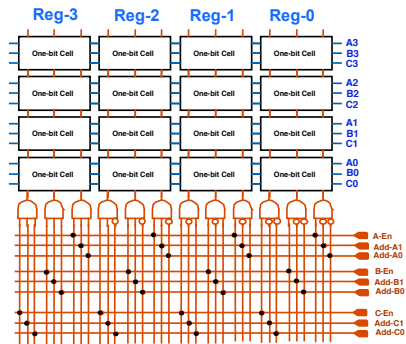

Summary

- Given Boolean function, generate a circuit that “realize” the function.
- Constructed circuits that can **add** and **subtract**.
- The **ALU**: a circuit that can **add**, **subtract**, **detect overflow**, **compare**, and do **bit-wise operations (AND, OR, NOT)**
- Shifter
- Memory Elements: **SR-Latch**, **D Latch**, **D Flip-Flop**
- **Tri-state drivers & Bus Communication**
- Register Files
 - ALU, Shift, Register Read/Write